



**MARA UNIVERSITY OF TECHNOLOGY
PENANG**

DEPARTMENT OF ELECTRICAL ENGINEERING

FINAL REPORT DIPLOMA PROJECT

TITTLE:

TO ADD HOURLY CHIME TO THE DIGITAL CLOCK

PREPARED BY:

MOHD. ZAMANI BIN ABDUL RAHMAN (KE 11)

95461970

MOHD. JAMIL BIN MOHD. ZAIN (KE 11)

95720823

DATE SUBMITTED:

30 OCTOBER 1999

SUPERVISOR:

MR. ALI BIN OTHMAN

ABSTRACT

This project is about an hourly chime that will add to your own digital clock. It is made to your clock looked more functional.

This project clock is using some common IC s and other active and passive components. In addition, from these components that have been used, we can learn more about the function of the components itself.

The price to make this project is a low cost hourly chime that is has 16 different tone that can enhance the charm of your digital clock. This unit can be attached equally well to clocks made using different clock IC s or any discrete IC chips.

And after we had finished this project, we have learned how to make our own chime that will add to the digital clock.

Finally, from this project, it can help us to improve our knowledge in the electronic components that always been used in the engineering world.

ACKNOWLEDGEMENTS

Firstly, we want to say thank you to Almighty Allah which have give to us strength and time in finishing this project report. We have learned many things in living when we are doing this project.

We are grateful to all those who evaluated the project report and give a good cooperation to us. Thank you to our supervisor, Mr. Ali Bin Othman whose has given us much information that has been used in this report.

We are also greatly indebted to several of our friends for sharing their ideas into this project. We also want to thank to any other people for helping us to make this report process bearable.

Thank you, so much.

TABLE OF CONTENTS

1.0	Introduction	4
2.0	Principle of the system	
2.1	Circuit diagram	5
2.2	Components list	6
2.3	Operation of the circuit	7
3.0	Integrated circuit and other devices	
3.1	IC 7404, Hex inverter	10
3.2	IC 7805, Voltage regulator	11
3.3	IC 7408, Quad-two-input AND gate	12
3.4	IC 74121, Monostable multivibrator	13
3.5	NE 555, Timer IC	14
3.6	IC 7493, Divide-by-16-counter	16
3.7	Bipolar transistors	17
3.8	Capacitors	18
3.9	Resistors	18
4.0	Project planning	
4.1	Printed Circuit Board (PCB) design	19
4.2	Costing	23
4.3	Time management	24
4.4	Gantt chart	25
5.0	Hardware development	26
6.0	Future recommendation	26
7.0	Conclusion	27
8.0	References	28
9.0	Appendices	
	Data sheets	Appendix A
	Resistor color code	Appendix B
	Semiconductor prefixes	Appendix C

1.0 INTRODUCTION

This project is started by introducing some underlying concepts that are important in the technologies.

The heart of this project is the interface and decoder. This part is one of the parts in the circuit. This circuit can be divided by three main parts.

The first part which is has 7404, 7408 and 7805 is called 7-segment to one decoder. It used to decode the output from the 7-segment of the clock.

The second part which have 74121 is called monoshot and driver circuit. It triggers the input and monoshots the output.

Lastly, the third part is musical tone generator circuit, which have 555 and 7493. This part is to generate the tone of the circuit. But, if any change to the tone, select the suitable component in this part and change it.

This project is also introduced some of the terminology that is necessary when embarking on a new field of study. More concepts will be expended on, as you are needed later in this project.