

UNIVERSITI TEKNOLOGI MARA
KAMPUS BUKIT MERTAJAM
2005

FINAL REPORT OF DIPLOMA PROJECT

FACULTY OF ELECTRICAL ENGINEERING



AC TO DC CONVERTER

ERWANAS ASMAR ISMAIL

SAIFUL BUHAIRIE MOHAMAD ADNAN

ACKNOWLEDGMENT

This project was made possible by the efforts and talents of many people. First of all, we would like to express our gratitude to God Almighty, with His blessing and love; we managed to complete our project.

Our sincerest appreciation must be extended to our project supervisor En. Mohammad Adha b. Mohammad Idin for all the help, guidance and patience during the process of completing this project. Not forget, Puan Shahilah binti Nordin, our project coordinator, who gives some advices and a valuable assistance. To all our friend and senior for give their hard work and contribution in giving ideas and supports. We would like to thank to our parent for their morale support that has built our spirit in completing this project. In times like these, we need a morale support due to burden that we had carried caused by other project report need to be submitted.

Finally we would like to thanks our group members for bearing with us during the research process and sharing their precious idea whilst we try to complete this proposal for the subject PROJECT 1 (KEU280 & KEU 380).

ERWANAS ASMAR

&

SAIFUL BUHAIRIE


UNIVERSITI TEKNOLOGI MARA

CAWANGAN PULAU PINANG

-- FEBUARY 2005

ABSTRACT

AC to DC converter using rectifier

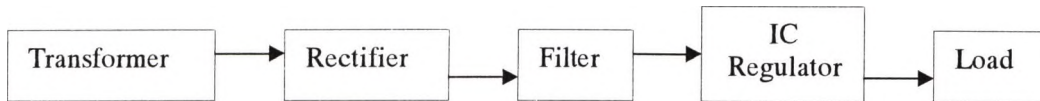

An AC/DC converter is actually a rectifying circuit which converts an alternating current into a pulsating DC voltage which is a unidirectional current. A rectifier circuit allows currents to flow only in one direction.

In other words, a rectifier is capable of converting a sinusoidal waveform (whose average value is zero), into a unidirectional waveform, whose average value is non-zero. There are two types of rectifiers, half-wave rectifier and full-wave rectifier. But to gain a much more improved DC level obtained from a sinusoidal input, AC/DC converter is very useful where its application has been used world wide. This is because of its capability of converting AC to DC, where most of sources that are being transmitted to users are in the form of AC. This is where the converter becomes an important tool to convert the AC to DC.

This report will describe how the AC/DC converter is implemented in daily use and works by using the Circuit Maker program.

TABLE OF CONTENTS

PAGE

Acknowledgement

Abstract

1. INTRODUCTION

1.1	Background	1
1.2	Scope of work	2
1.3	Objective of project	6

2. TECHNIQUES CONVERTER

2.1	Half wave rectifier	7
2.2	Full-wave centre tapped rectifier (FWCT)	8
2.3	Full-wave bridge rectifier (FWB)	9

3. CIRCUIT DESIGN AND OPERATION

3.1	Circuit design	
	3.1.1 Schematic diagram	10
	3.1.2 Component list and data	10
3.2	Circuit simulation	
	3.2.1 Circuit maker software	18
	3.2.2 Simulation procedure	19

CHAPTER 1

INTRODUCTION

1.1 Background

What is the function of rectifier? The rectifiers used to convert the alternating current (AC) to direct current (DC). The connection of diodes can be done in many ways diodes to. The bridge rectifier is the most important and it produces full-wave varying DC. A full-wave rectifier can also be made from just two diodes if a centre-tap transformer. Rectifier that using 2 diodes and requires a center-tapped transformer to establish the input signal across each section of the secondary of the transformer. The output will perform a DC voltage according to the circuit. When input voltage produce positive cycle, D1 will short circuit while D2 will open circuit. This will produce the output wave a positive wave. And when negative cycle is produce from the source, D1 and D2 will vice-versa. The output will keep on producing positive wave and hence, DC voltage can be generated from this circuit.

Filtering is performed by a large value electrolytic capacitor connected across the DC supply to act as a reservoir, supplying current to the output when the varying DC voltage from the rectifier is falling. The diagram shows the unsmoothed varying DC (dotted line) and the smoothed DC (solid line). The capacitor charges quickly near the peak of the varying DC, and then discharges as it supplies current to the output.

A voltage regulator (or voltage regulator IC units, LM7809) is used to maintain a constant output voltage. A voltage regulator also can use DC input to provide a DC voltage that not only has much less ripple voltage but remain the same DC value even if the input DC voltage varies somewhat, or the load connected to the output DC voltage changes. Voltage regulators are very robust. They can withstand over-current draw due to short circuits and also over-heating. In both cases the regulator will shut down before damage occurs. The only way to destroy a regulator is to apply reverse voltage to its input. Reverse polarity destroys the regulator almost instantly.