## A VOICE OPERATED RELAY

A project report presented in partial fulfillment of the requirement for the award of Diploma in Electronic Engineering of MARA-Institute of Technology

Bv:

NOR HASNAH BIE HAJI HASSAN

DEPARTMENT OF ELECTRONICS ENGINEERING

MARA INSTITUTE OF TECHNOLOGY

SHAH ALAM 40450 SELANGOR

#### ABSTRACT

Voice Operated Relay is actually a device allows virtually hand-free operation of the radio. It sampled the sound from a microphone and switched a relay when the level of the microphone exceed the preset level. The relay is held on as long as the sound level stays above that threshold and when the microphone drop below the critical level the relay are. off.

This report covered all the circuit operation. The explaination is made simpler by using the block digram before going into detail in term of circuit digram.

Since the aim of the project is to familiaries the student with the various application of electronic circuit theory, device and circuit component, an explaination on circuit theory are also included. Finally, suggestion for futher inprovement are also given.

# ACKNOWLEDGEMENT

In completing this project, I wish to express great indebtedness to my project advisor Mrs. Kamariah Ismail for her very kind guidances, useful and constructive critism and suggestions. Also I am greatful to all laboratory technicians and friends who have willingly help me in many ways.

## TABLE OF CONTENT

	Page
Abstract	i
Acknowlegement	ii
Table of Content	iii
List illustration and figtures	<b>v</b>
Nomenclature	vi
CHAPTERS	
1. INTRODUCTION	1
2. SYSTEM OPERATION	3
2.1.1 Non-inverting Amplifier	3
2.1.2 Differentiating Amplifier	7
2.1.3 Switching Transistor	8
2.1.4 Voltage Devider	12
2.1.5 Single Pole Double Throw Relay	. 12
3. THE CIRCUIT SYSTEM	15
4. CONSTRUCTION OF THE PROJECT	17
4.1 Requirement	18
4.1.1 Procedure	18
4.2 Etching Process	19
4.3 Construction	19
4.4 Assembly	19
5. ADJUSTMENT AND OPERATION	23

# TABLE OF CONTENT (con't)

6. 7.	DISCUSSION AND COMMENTS CONCLUSION	************	25 27
12			360
	REFERENCES	*************	28
12 <sup>2</sup> 281 2	APPENDICES	***********	29