# THE LONG DURATION TIMER

PROJECT REPORT KEU 380 DIPLOMA IN ELECTRICAL ENGINEERING FACULTY OF ELECTRICAL ENGINEERING MARA UNIVERSITY OF TECHNOLOGY PULAU PINANG



## MARA UNIVERSITY OF TECHNOLOGY

Prepared by:

MOHD FAIZAL BIN MOHD SALEH & ZAINUDI BIN ABDUL WAHAB

JUN-NOVEMBER 1999

MARA UNIVERSITY OF TECHNOLOGY

## MARA UNIVERSITY OF TECHNOLOGY

### **PULAU PINANG**

A report submitted to the faculty of electrical engineering, Mara University of Technology in partial

fulfillment for the Diploma in Electrical Engineering

ZAINUDI B. AB. WAHAB )

96237320

KE 11

(MOHD FAIZAL B. MOHD SALLEH)

96237313

KE 11

#### **APPROVED BY**

(MR. DEBNATH. NIRANJAN)

PROJECT SUPERVISOR

#### ACCEPTED BY

( PN. NOORITAWATI MAT TAHIR )

COORDINATOR OF ELECTRICAL ENGINEERING

## ACKNOWLEDGMENT

In the name Allah (s.w.t ) the most gracious and merciful. Thank to allah (s.w.t) for giving us opportunity complete this KEU 280 project paper although we have some problem to complete it succesfully.

We would like to express our deep sense of gratitude and appreciation to our project advisor Mr. Debnath Niranjan and our coordinator Pn. Nooritawati for their consistent advise and guidance as well as provision of their valuable time, encouragement and patience during the period of completing this project.

We are also grateful to all staff members of the computer laboratory for their support and technical expertise a special thank to Mr. Ahmad ismail for his ever enduring support during the duration of the project.

We are very grateful both our advisor and we will never forget everything, especially their cooperation for us and we appreciate it a lot.

Finally we would like to express our deepest gratitude to our family and friends for their unlimited encouragement. They have all been a constant source of strength and inspiration to us.

Thanks, wassalam.

## ABSTRACT

All praise to be ALLAH, the Sustainer of the worlds; and blessing and peace be upon our leader and chief, Nabi Muhammad S.A.W, upon his companions, and upon those who followed them with sincerity until the Day of Judgement.

In today's world, the term digital has become part of our everyday vocabulary because of dramatic way that the digital circuit and digital techniques have become so widely used in almost all areas of live: Computers, automation, robot, medical science and technology, transporting, space exploration and others.

Currently we live in an information age. During everyday of our live, we are provided with a tremendous access to worldwide events. Some of this information, which is received by our sense (sight, sound, etc..) is conditioned, analyzed and finally the brain processes it. For example, light energy is continuously received in this energy is converted into another form and finally it is processed by the brain. The brain than changes the information into a form that can be more easily stored and analyzed.

In electronic, it is very useful to represent or code information such as voltage or current into another form, referred to as digital, as indicated, a brain code into a form, referred to as advantage to analyze and storage. Similarly, the coding of information into a digital code provides a powerful tool to analyze and design a wide range of a complete electronic circuit and system because of their ability to process information quickly.

Digital logic is used in almost every product and technology. For example we took our project, were our project can setting the time we needed at the digital audio and videos by just switch the range of setting time using a IC timer. The output will come out into the LED digital display and oscillator. This project also using some component likes transistor, capacitor and resistor. This can make easy work and comfortable.

ACKNOWLEDGEMENT	i
ABSTRACT	ii
INTRODUCTION	1
1.1 CONCTRUCTION	1
1.2 555 ASTABLE & MONOSTABLE	2-3
2.0 BINARY ( + 16 ) COUNTER	4-5
3.0 CAPACITOR	6
3.1 DEFINATION & DESCRIPTION OF CAPACITOR	6
4.0 RESISTOR	7
4.1 USES & TYPES	7
OPERATING PRINCIPLE	8-9
5.2 CALIBRATION	10
6.0 WORKING SEQUENCE	11-12
7.0 TESTING CIRCUIT	13
7.1 OUTPUT WAVEFORM FROM IC1, IC2 & IC3	13
8.0 THE BAR CHART PLANNING	14
8.1 THE GANTT CHART	15
9.0 DISCUSSION	16
10.0 CONCLUSION	17
11.0 REFERENCE	18